

## Optional Verilog Assignment


**Objective :** RTL (Register Transfer Level) Simulation of a Serial Multiplier

**Multiplier:** The multiplication algorithm is ‘repeated addition’ as described below:


```

IF { Start = 1} Then
    Read A, B;
    Done←0;
    Temp←0;
    WHILE(A > 0) Loop
        A ←A-1;
        Temp←Temp+B;
    END WHILE
    Z←Temp;
    Done←1;
ENDIF ;


```

 


The RTL block diagrams are shown below:

 


Multiplier

 


Datapath

 


 

 
```
module adder4 (A,B,S);
/* Structural code given
using 1 bit Fulladder made
in verilog Lab */
```



 
```
module Reg4 (Din,Rst,Clk,LD,Dout);
/* Write behavioral code */
```



 
```
module mux4 (A,B,sel,Y);
/* Write behavioral code*/
```


 
```
module dec4 (A, Y);
/* Structural Code given*/
```



 
```
module or4 (A,r);
/*This essentially keeps
count of the number of
steps. Think carefully
when should r become zero,
and write the code */
```



```
module datapath(A,B,Clk,Rst,CW,r,Z);
/* Combine all these modules together*/
```


The Controller is a Mealy state machine.

 

$CW[0] = LD_1 ; CW(1)=LD_2 ; CW(2)=LD_3 ; CW(3) = LD_4 ; CW(4) = Sel1 ; CW(5) = Sel2 .$

$CW1 : 6'b000000 ; CW2 : 6'b000111; CW3 : 6'b110101; CW4 : 6'b001000$

 Combine the datapath and controller to create a new entity mult.v



1. Simulate the multiplier and verify its operation using a testbench test\_mult.v.
2. Put all the verilog files in a single folder, zip it and mail it to [veeramani@gmail.com](mailto:veeramani@gmail.com) with the subject “[EE summer camp] Opt Verilog”.
3. You may mail us as soon as you finish, but not later than 8 AM, 20<sup>th</sup> May.
4. This assgmt is compulsory for those who want to take a project in Computer Architecture.

## Verilog Files

### adder4.v

```
module adder4 (A,B,S);
  input [3:0] A,B;
  output [3:0] S;
  wire [3:0] S;
  wire [3:0] temp;

  fulladder      adder1_1 (A[0],B[0],1'b0,S[0],temp[0]);
  fulladder adder1_2 (A[1],B[1],temp[0],S[1],temp[1]);
  fulladder adder1_3 (A[2],B[2],temp[1],S[2],temp[2]);
  fulladder adder1_4 (A[3],B[3],temp[2],S[3],temp[3]);
  /* Alternate style :
   * fulladder adder1_1
   * (.a(A[0]),.b(B[0]),.cin(1'b0),.sum(S[0]),.cout(temp[0]));
   * Here the “.” refers to original arguments specified in the 1 bit
   * full adder file. They are not necessary to be used, however, this
   * style is considered better.
   */
endmodule
```

### dec4.v

```
module decr4 (A, Y);
  input [3:0] A;
  output [3:0] Y;
  wire [3:0] Y;
  wire [3:0] C;
  assign C[0]=1'b0;
  assign C[1]=(A[0] | C[0]);
  assign C[2]=(A[1] | C[1]);
  assign C[3]=(A[2] | C[2]);
  assign Y[0]=(~(A[0]) ^ C[0]);
  assign Y[1]=(~(A[1]) ^ C[1]);
  assign Y[2]=(~(A[2]) ^ C[2]);
  assign Y[3]=(~(A[3]) ^ C[3]);
endmodule
```

**controller.v**

```
`define s0    1'b0
`define s1    1'b1

module controller(clk,r,start,done,CW);
input clk,r,start;
output done;
reg done;
output [5:0] CW;
reg [5:0] CW;

reg state;

always @(posedge clk) begin
  if (start == 0)
    state <= `s0;
  else begin
    if (state == `s0)
      state <= `s1;
    else if (r == 1'b1)
      state <= `s1;
    else
      state <= `s0;
  end
end

always @(state,r,start) begin
  if (state == `s0 ) begin
    if (start == 0) begin
      CW <= 6'b000000;
      done <= 0;
    end
    else begin
      CW <= 6'b000111;
      done <= 0;
    end
  end
  else if (state == `s1) begin
    if (r == 1) begin
      CW <= 6'b110101;
      done <= 0;
    end
    else begin
      CW <= 6'b001000;
      done <= 1;
    end
  end
end
end

endmodule
```